

POWER-TUNE THE PHYSICS OF ITS WORKING PRINCIPLE EXPLAINED

By: Dr Ir Amir Basha Ismail

A. Introduction

- The power-tune is essentially power factor capacitive element equipment for improving the load power factor of a normally inductive load.
- It essentially provides a leading current injection phasor into the normally lagging inductive loads that are characteristic of electrical loads present in the household.
- A household power point (13A) distribution circuit normally has three (3) 13A power-point socket outlets connected in parallel, as shown below.
- The first power point in the distribution circuit would be the best point for connecting the power-tune, as shown below in Figure 1.

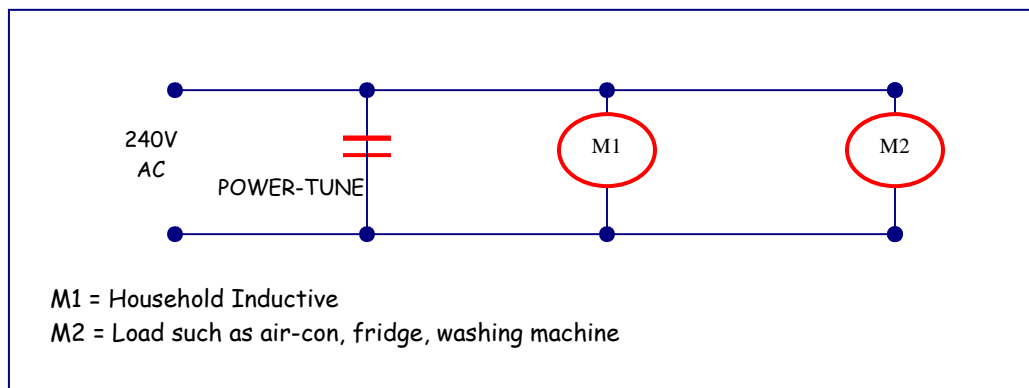


Figure 1: Illustrating the Concept

B. Example of Calculation to Demonstrate the Physics of Working Principle

- Two air-conditioning loads, M1 and M2 each rated at 1.5hp and 2.5hp are connected as shown above.
- Say, the two air-cons have an efficiency of 84% (η) and a power factor of 0.8 lagging. We lump the two air-con loads as an equivalent load of 4hp, called M.

POWER-TUNE THE PHYSICS OF ITS WORKING PRINCIPLE EXPLAINED

By: Dr Ir Amir Basha Ismail

- c. First, we need to calculate the input volt amperes, as such:

$$\eta = \frac{\text{output power (Watts)}}{\text{input power (Watts)}} = \frac{4 \times 786}{IV \times pf}$$

$$IV = \frac{2984}{0.8 \times 0.84} = \frac{2984}{0.672}$$

$$= \mathbf{4440 \text{ VA}}$$

- d. Next, we calculate the current taken by the motor of the lumped air-con load (M) of 4hp, i.e.

Current taken by M:

$$I_m = \frac{\text{Input volt-ampere}}{\text{Voltage}} = \frac{4440}{240} = \mathbf{18.5 \text{ Amps}}$$

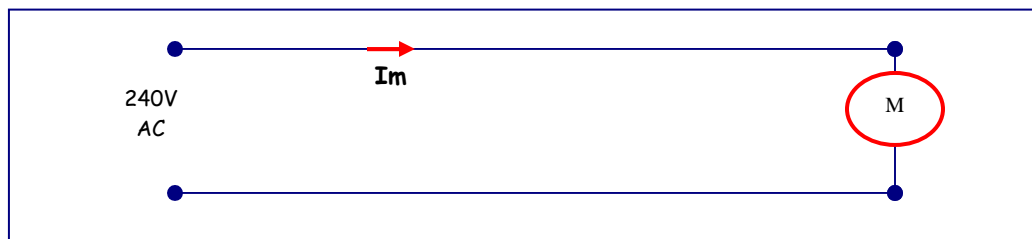


Figure 2: Circuit Diagram without insertion of Power Tune

- e. Now, if we place the power tune (capacitance) in the first power point outlet of the power distribution circuit as shown in Figure 1, the circuit diagram becomes as shown below in Figure 3. The respective electrical phasor diagram is as shown in Figure 4.

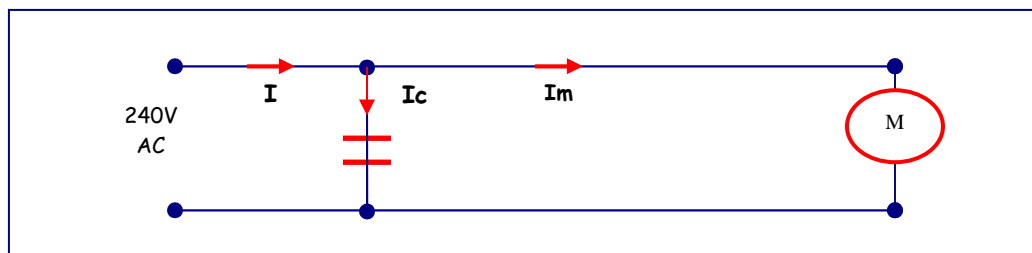


Figure 3: With Power Tune in Circuit ($I = I_c + I_m$)

POWER-TUNE THE PHYSICS OF ITS WORKING PRINCIPLE EXPLAINED

By: Dr Ir Amir Basha Ismail

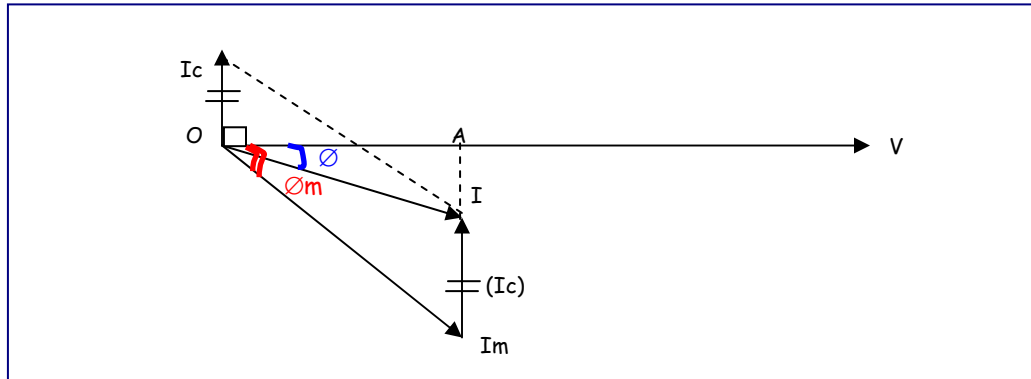


Figure 4: Electrical Phasor of Figure 3

- f. Say, by placing the power tune, the power factor of the motor (M) is raised to 0.92 from 0.8 ($\cos \varnothing_m$)
- g. Current I_c taken by the power tune must be such that when combined with I_m , the resultant current I lags the supply voltage V by an angle \varnothing , where $\cos \varnothing = 0.92$.

From Figure 4,

$$\text{Active component of } I_m = I_m \cos \varnothing_m = 18.5 \times 0.8 = 14.8 \text{ Amps (OA)}$$

And

$$\text{Active component of } I = I \cos \varnothing = I \times 0.92 \text{ (OA)}$$

- h. This component are represented by OA as in Figure 4,
Hence,

$$I \times 0.92 = 14.8$$

$$I = 14.8 / 0.92 = 16.09 \text{ Amps}$$

- i. Reactive component of $I_m = I_m \sin \varnothing_m = 18.5 \sin \varnothing_m$, where \varnothing_m is $\cos^{-1} 0.8 = 36.9^\circ$, and therefore $\sin \varnothing_m = 0.6$, leading to reactive component of

$$I_m = 18.5 \times 0.6 = 11.1 \text{ Amps} \longrightarrow \textcircled{1}$$

POWER-TUNE THE PHYSICS OF ITS WORKING PRINCIPLE EXPLAINED

By: Dr Ir Amir Basha Ismail

- j. Reactive component of $I = I \sin\phi = 16.09 \sin\phi$, where ϕ is $\cos^{-1} 0.92 = 23.0^\circ$, and therefore $\sin\phi = 0.39$, leading to reactive component of

$$I = 16.9 \times 0.39 = 6.30 \text{ Amps} \longrightarrow \textcircled{2}$$

- k. Thus, from Figure 4 (of the phasor diagram) it will be seen that:

$$I_c = (\text{reactive component of } I_m) - (\text{reactive component of } I)$$

$$I_c = 11.1 - 6.3 = 4.8 \text{ Amps} \longrightarrow \textcircled{3}$$

- l. Capacitive Reactance (X_c):

$$X_c = \frac{1}{W_c} = \frac{1}{2\pi f C}$$

$$I_c = V / X_c$$

$$I_c = 2\pi f C V$$

$$4.8 = 2 \times 3.142 \times 50 \times C \times 240$$

$$\text{Therefore, } C = 63.65 \mu\text{F}$$

- m. From the above calculations, it will be seen that the effect of connecting the $63.65\mu\text{F}$ capacitor (Power -Tune) in parallel with the household loads of air-con is to reduce the current taken from the supply from 18.5A to 16.09A without reducing/altering the current taken or power taken by motor/loads.

POWER-TUNE THE PHYSICS OF ITS WORKING PRINCIPLE EXPLAINED

By: Dr Ir Amir Basha Ismail

C. Conclusions

- a. The calculations (as illustrated in this Paper with the aid of electrical phasor diagram) demonstrate the physics of the working principle of the so-called "Power-Tune", which is essentially power factor correction capacitor equipment.
- b. The Power-Tune effectively reduces the current taken from the utility supply by a certain amount depending on the capacitor size of the equipment. Hence, a reduction in energy (kwh) consumption in the household fitted with the device.
- c. It essentially provides a leading current injection phasor into the normally-lagging electrical loads.
- d. For the illustrated case, an improvement in the power factor of 15% (i.e. from 0.80 to 0.92) results in 13% reduction in utility supply current (i.e. from 18.5A to 16.09A)
- e. There is NO reduction in current / power taken by load themselves.
- f. The equipment should be fitted "in front" of the inductive loads (such as air-cons, fridge, washing machine, etc.) in the power distribution circuit.